

DIGITAL LOGIC AND DESIGN

LAB ASESSMENT – 4

Name: **VIBHU KUMAR SINGH**

Reg. No: **19BCE0215**

Teacher: **Sairabanu J.**

EXPERIMENT 5:

Q1) Design a 4-bit Binary parallel Adder.


A1)

AIM:

To design a 4-bit Binary Parallel Adder.


DESIGN:

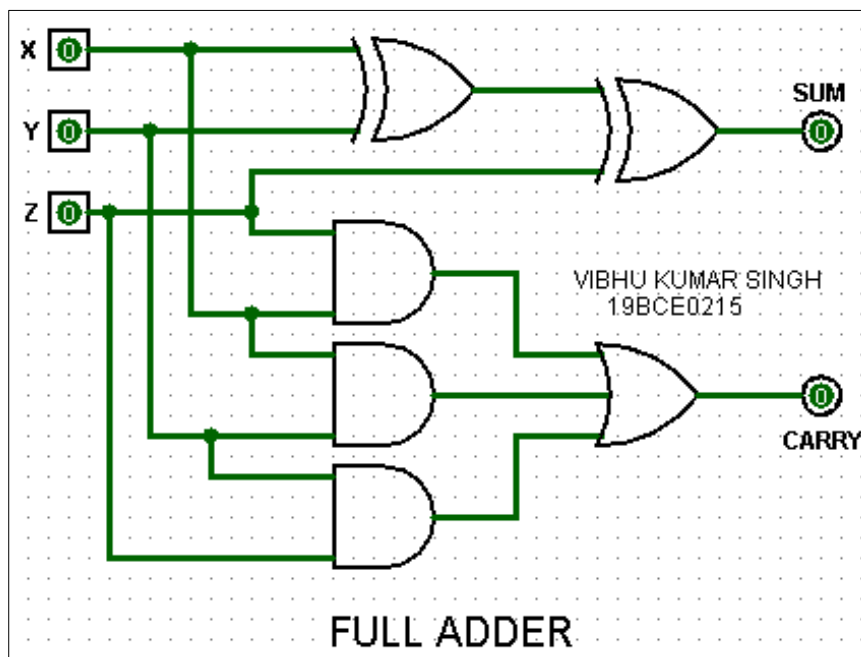In order to make 4-bit Binary Parallel Adder, a single Full Adder circuit is saved as user I.C. and imported in another Logisim file to make Binary Parallel Adder. The circuit for Full Adder is:



FULL ADDER					
INPUT			OUTPUT		
X	Y	Z	Sum	Carry	
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	1	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

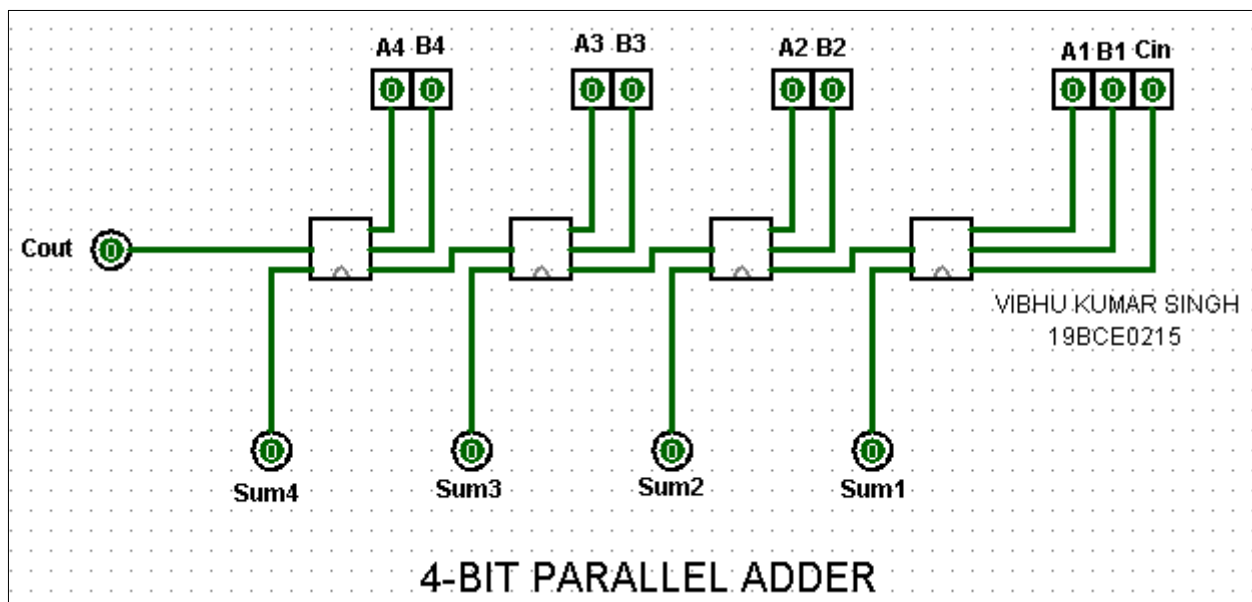This Full Adder circuit is saved as user I.C. and imported in another file. The circuit for 4-bit Binary Parallel Adder is:




SCREENSHOTS:

EXAMPLE 1:

A=1110 B=1010

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	1	1	0
+	1	0	1	0
1	1	0	0	0

OUTPUT 1:

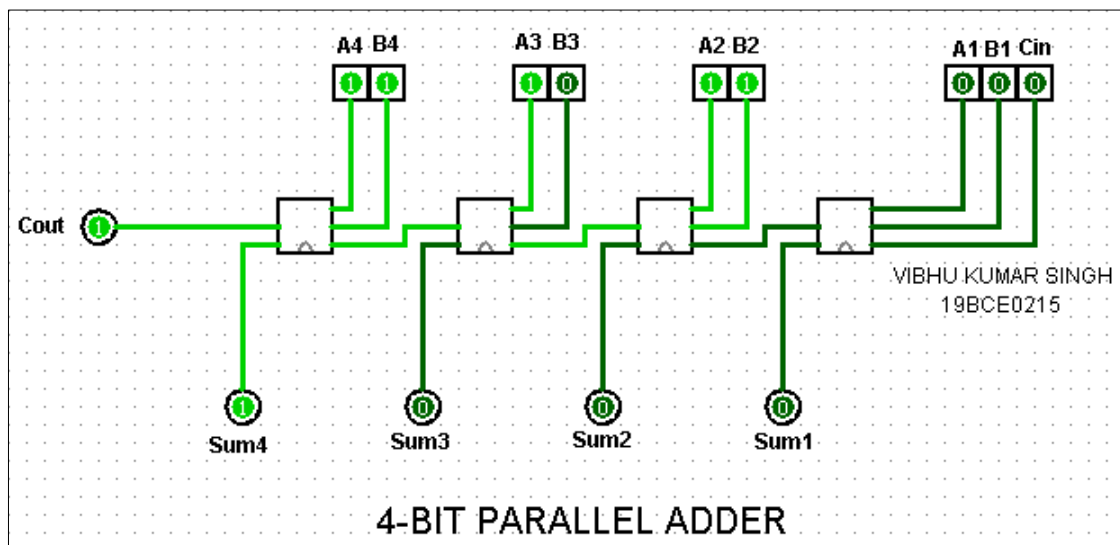


EXAMPLE 2:

A=1111 B=1011

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	1	1	1
+	1	0	1	1
1	1	0	1	0

OUTPUT 2:

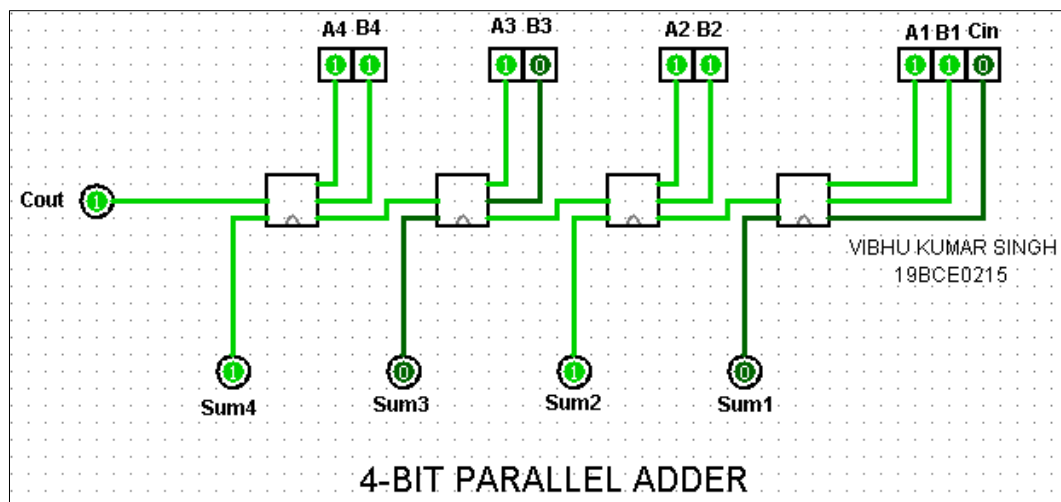


EXAMPLE 3:

A=0111 B=0011

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	0	1	1	1
+	0	0	1	1
	0	1	0	1

OUTPUT 3:

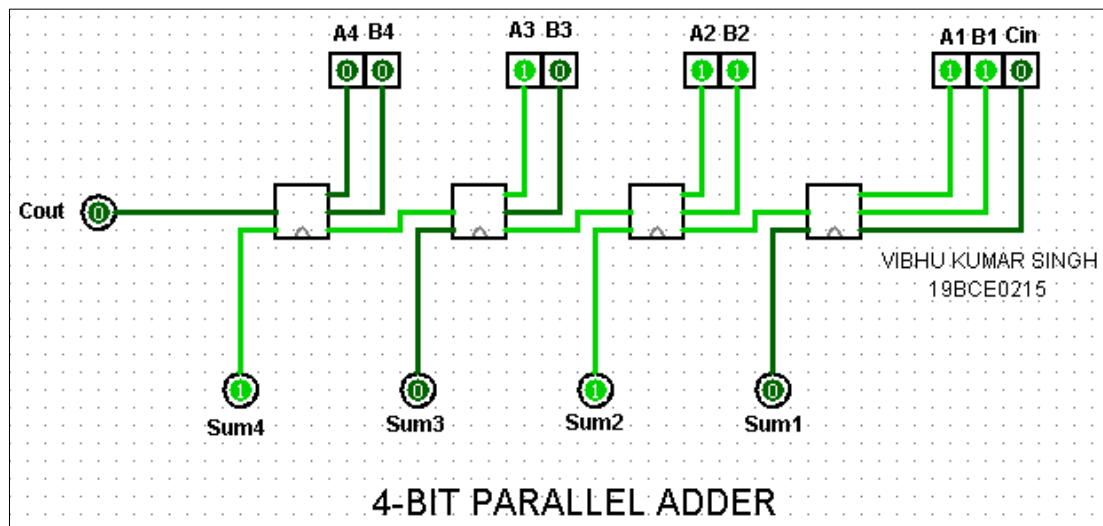


EXAMPLE 4:

A=1000 B=1100

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	0	0	0
+	1	1	0	0
	1	0	1	0

OUTPUT 4:

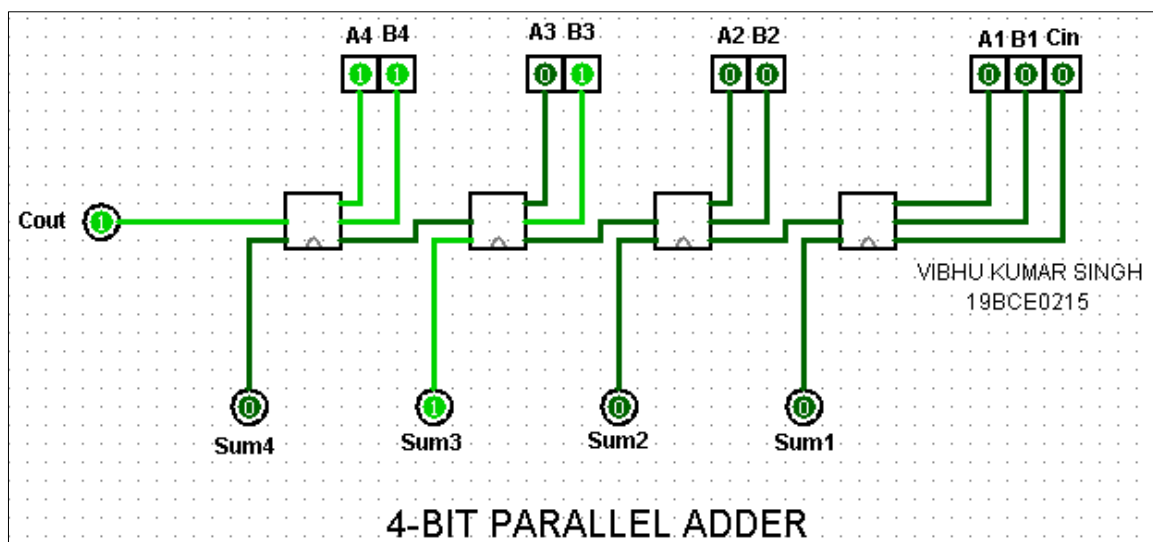

Q2) Design Excess 5 to BCD using Binary parallel adder.


A2)

AIM:


To design Excess 5 to BCD using Binary Parallel Adder.

DESIGN:

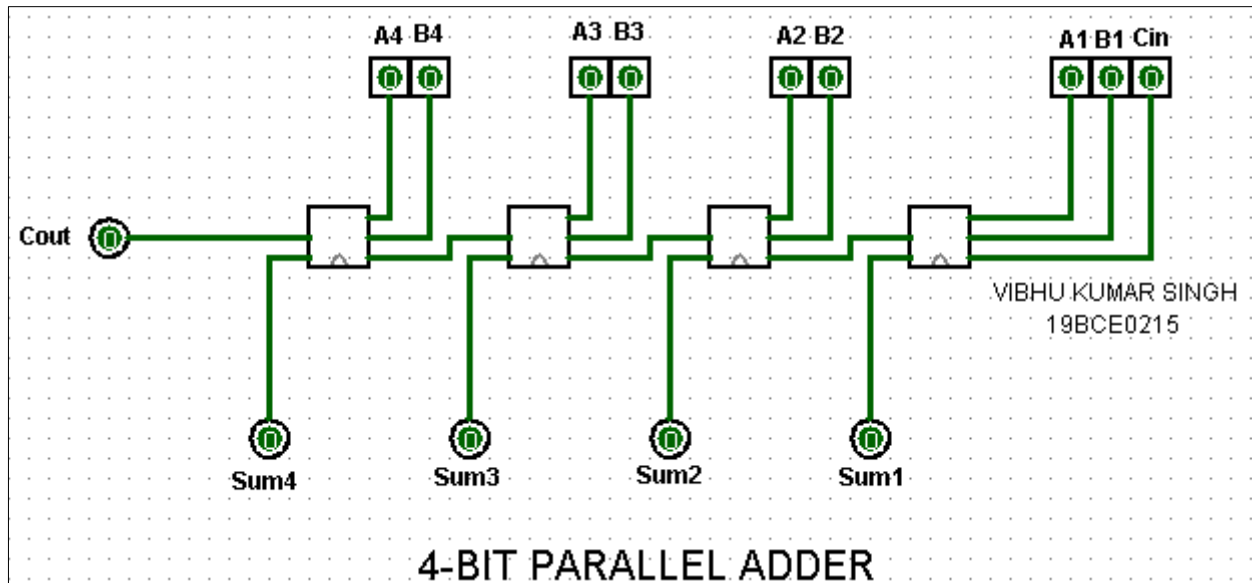It has the same principle as a regular 4-bit Binary Parallel Adder except we will be subtracting 5(0101) from the given BCD code using 2's complement subtraction i.e. add (1011). The circuit for Binary Parallel Adder is saved as user I.C. and imported in a new Logisim file. The circuit for Binary Parallel Adder is:



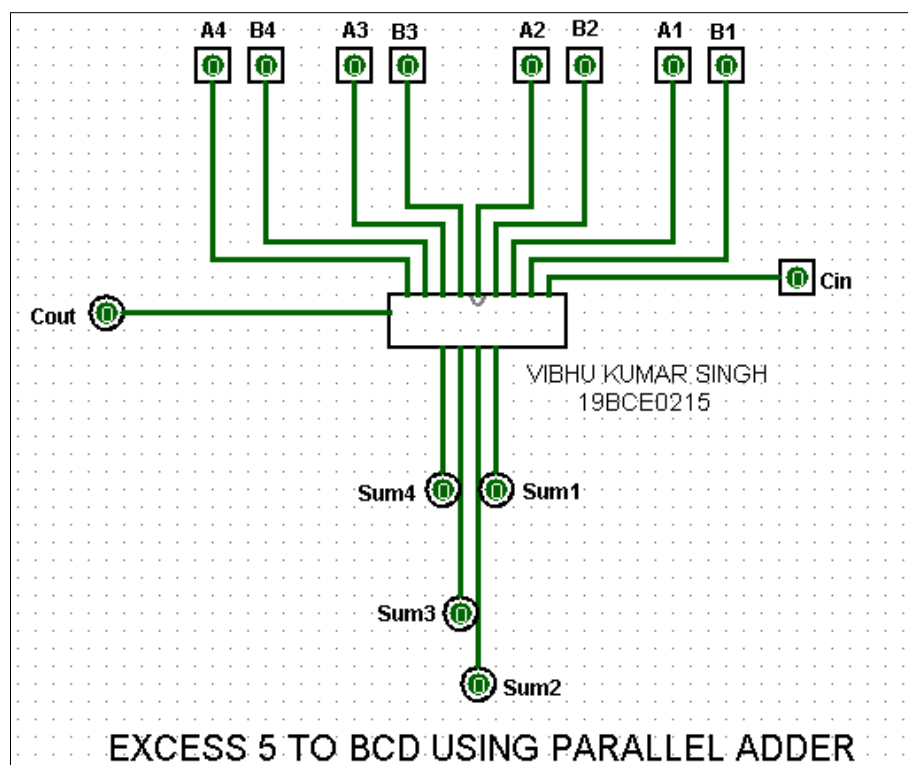This Binary Parallel Adder circuit is saved as user I.C. and imported in another file. The circuit for Excess 5 to BCD converter using Binary Parallel Adder is:



SCREENSHOTS:

EXAMPLE 1:


Convert A=1000 into BCD code.

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	0	0	0
+	1	0	1	1
	1	0	0	1

Since end carry is generated, it is discarded.

So, the BCD code is **0011**.

OUTPUT 1:

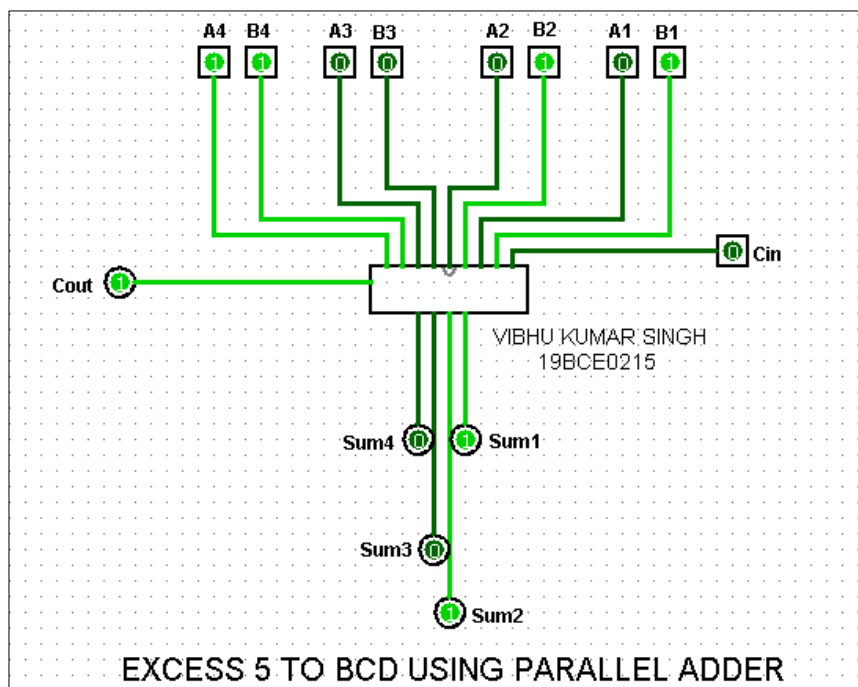

EXAMPLE 2:


Convert A=1001 into BCD code.

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	0	0	1
+	1	0	1	1
	1	0	1	0

Since end carry is generated, it is discarded.

So, the BCD code is **0100**.

OUTPUT 2:

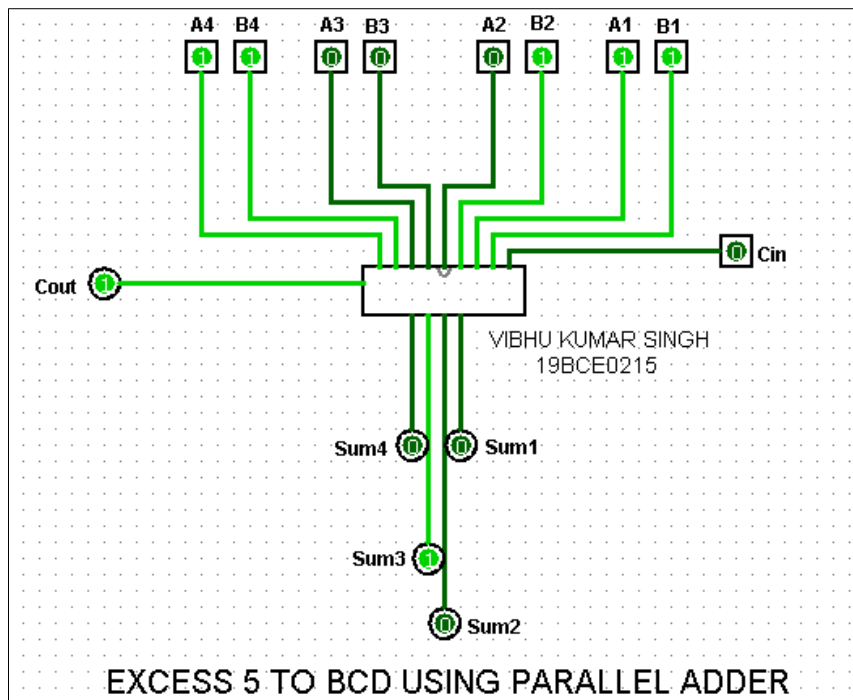

EXAMPLE 3:


Convert A=1010 into BCD code.

	A_4/B_4	A_3/B_3	A_2/B_2	A_1/B_1
	1	0	1	0
+	1	0	1	1
	1	0	1	1

Since end carry is generated, it is discarded.

So, the BCD code is **0101**.

OUTPUT 3:

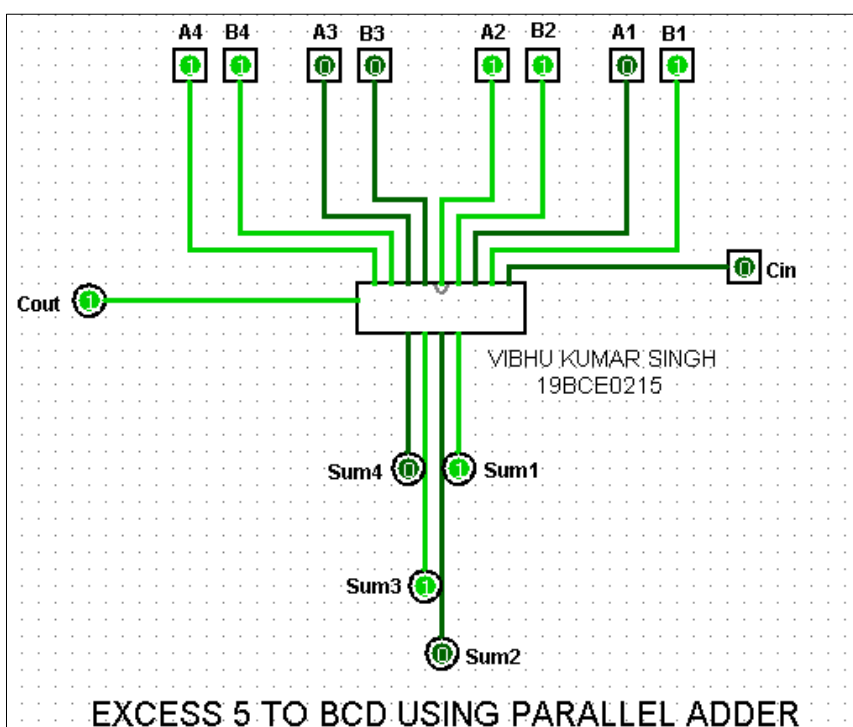


EXAMPLE 4:

Convert A=1011 into BCD code.

	A ₄ /B ₄	A ₃ /B ₃	A ₂ /B ₂	A ₁ /B ₁
	1	0	1	1
+	1	0	1	1
	1	0	1	0

Since end carry is generated, it is discarded.
So, the BCD code is **0110**.

OUTPUT 4:

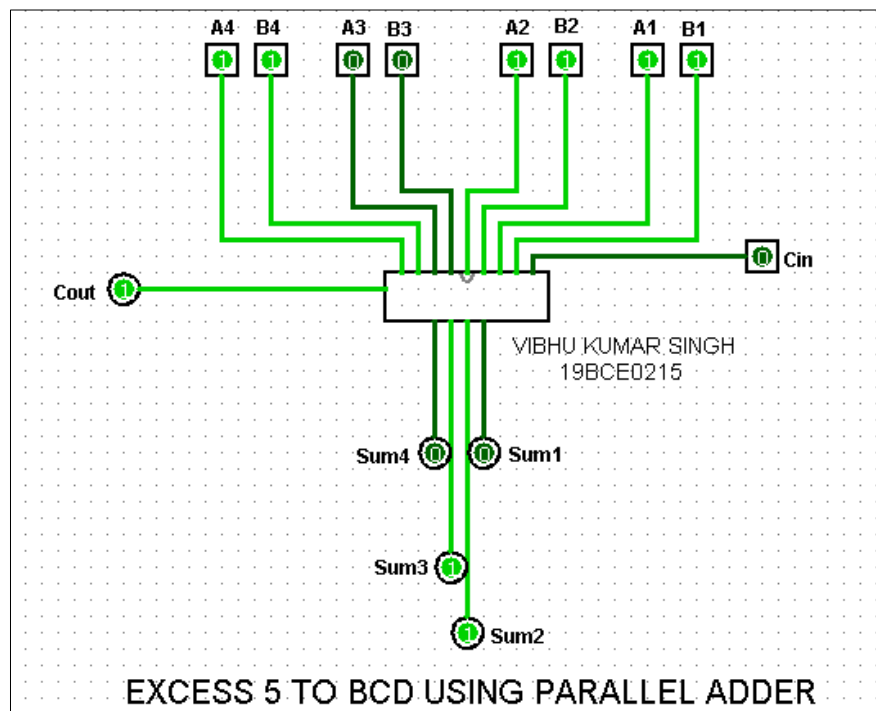

Q3) Design a 2-bit magnitude comparator.

A3)

AIM:

To design a 2-bit Magnitude Comparator.

TRUTH TABLE:

2-BIT MAGNITUDE COMPARATOR				
INPUT		OUTPUT		
A ₂ A ₁	B ₂ B ₁	A>B	A=B	A<B
0 0	0 0	0	1	0
0 0	0 1	0	0	1
0 0	1 0	0	0	1
0 0	1 1	0	0	1
0 1	0 0	1	0	0
0 1	0 1	0	1	0
0 1	1 0	0	0	1
0 1	1 1	0	0	1
1 0	0 0	1	0	0
1 0	0 1	1	0	0
1 0	1 0	0	1	0
1 0	1 1	0	0	1
1 1	0 0	1	0	0
1 1	0 1	1	0	0
1 1	1 0	1	0	0
1 1	1 1	0	1	0

BOOLEAN EXPRESSIONS:

- FOR (A>B):


$$=A_1.B_1' + X_1.A_0.B_0'$$
- FOR (A=B):

$$=X_1.X_0$$
- FOR (A<B):


$$=A_1'.B_1 + X_1.A_0'.B_0$$

DESIGN:

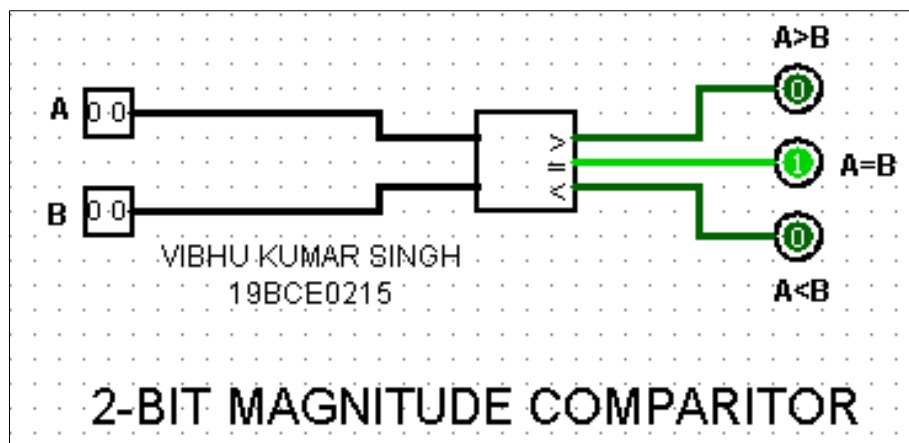
The circuit of 2-bit Magnitude Comparator is made using a predefined I.C. in Logisim. The circuit for 2-bit Magnitude Comparator is:




SCREENSHOTS(4):

 


2-BIT MAGNITUDE COMPARITOR

 

2-BIT MAGNITUDE COMPARITOR

 

2-BIT MAGNITUDE COMPARITOR

 

2-BIT MAGNITUDE COMPARITOR

Q4) Design a circuit to determine the greatest of 3 2-bit numbers using a 2 bit magnitude comparator.

A4)

AIM:

Design a circuit to determine the greatest of 3 2-bit numbers using a 2-bit Magnitude Comparator.

TRUTH TABLE:


2-BIT MAGNITUDE COMPARATOR					
INPUT				OUTPUT	
A ₂	A ₁	B ₂	B ₁	A>B	A=B
0	0	0	0	0	1
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	0	0
1	1	0	0	1	0
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	0	1

BOOLEAN EXPRESSIONS:


- FOR (A>B):
 $=A_1.B_1' + X_1.A_0.B_0'$
- FOR (A=B):
 $=X_1.X_0$
- FOR (A<B):
 $=A_1'.B_1 + X_1.A_0'.B_0$

DESIGN:

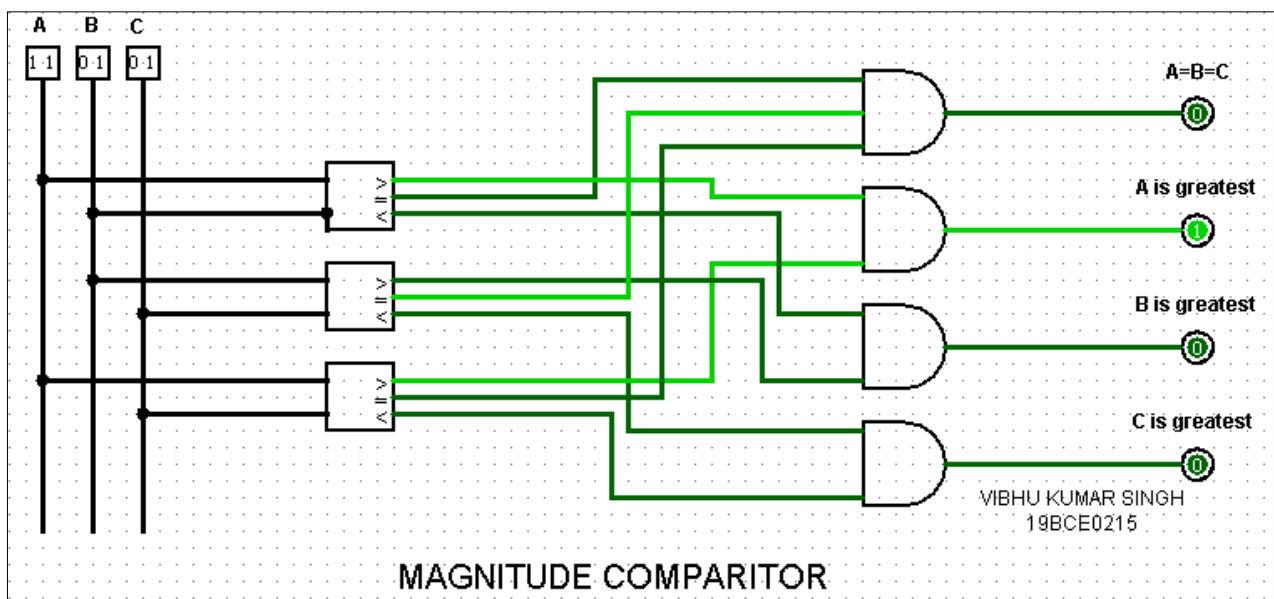Three 2-bit Magnitude Comparator I.C.(s) are used to determine the greatest of 3 2-bit numbers. The circuit is as follows:



SCREENSHOTS(4):

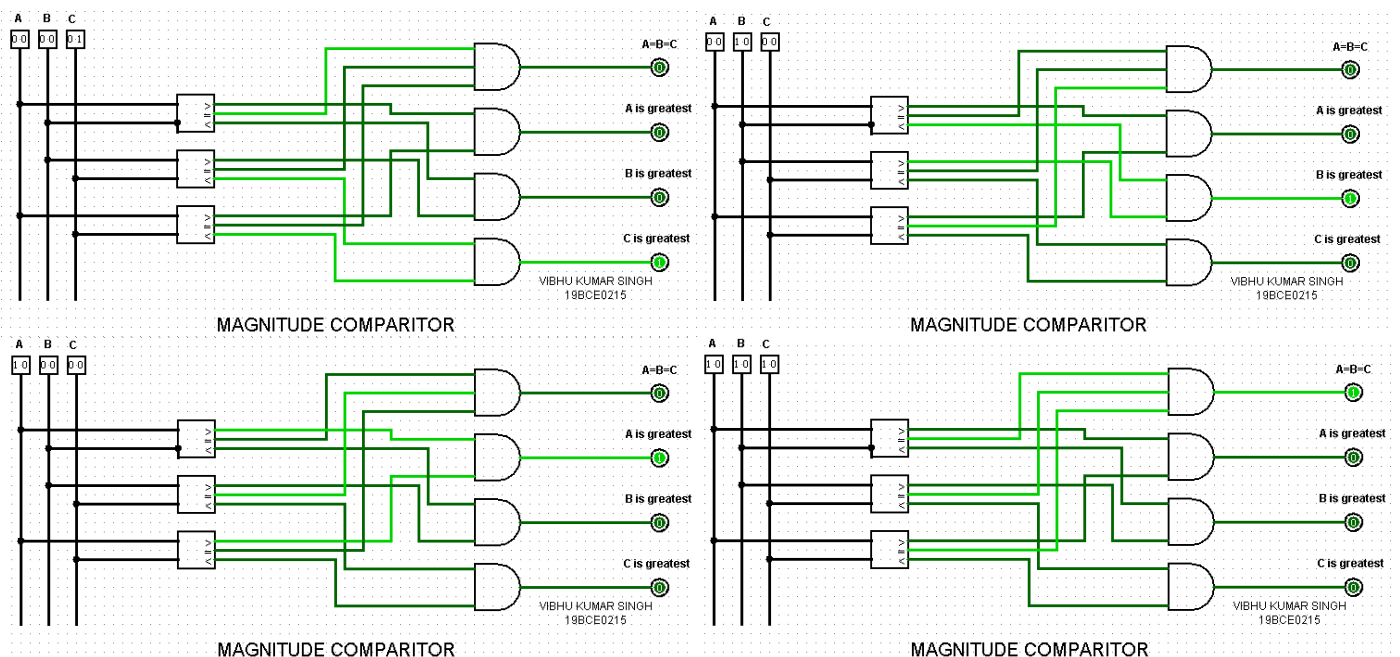

EXPERIMENT 6:

Q1) To design 2 to 4 line decoder using AND Gates.

A1)

AIM:

To design 2 to 4 line decoder using AND Gates.

TRUTH TABLE:

2-TO-4 DECODER					
INPUT		OUTPUT			
X	Y	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	1	0	1	0
1	1	0	0	0	1

BOOLEAN EXPRESSIONS:

$$D_0 = X'Y'$$


$$D_1 = X'Y$$

$$D_2 = XY'$$


$$D_3 = XY$$

DESIGN:

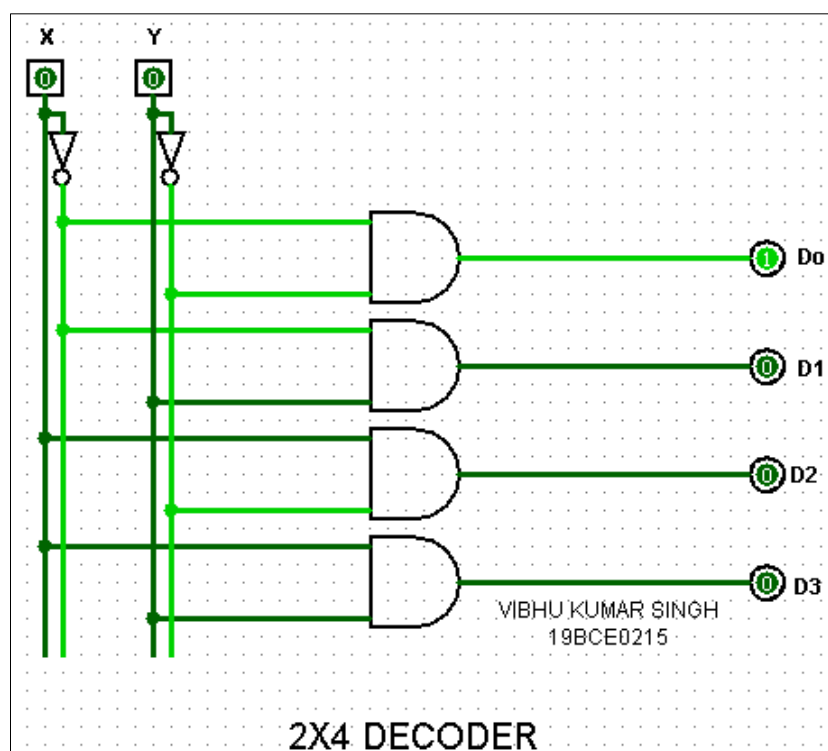
Using the above Boolean expressions, the Decoder can be made using basic AND Gates. The circuit for 2 to 4 line decoder is:




SCREENSHOTS(4):

 


2X4 DECODER

 

2X4 DECODER

 

2X4 DECODER

 

2X4 DECODER

Q2) Design a logic circuit to control the traffic light as per the given details. Vehicle detection sensors are placed along C and D (main road) and lanes A and B (access road). These sensor outputs are LOW (0) when no vehicle is present and HIGH (1) when a vehicle is present. The intersection traffic light is to be controlled according to the following logic:

- The east-west (E-W) traffic light will be green whenever both lanes C and D are occupied.
- The E-W light will be green whenever either C or D is occupied but lanes A or B are not occupied.
- The north-south (N-S) light will be green whenever both lanes A and B are occupied but C or D are not occupied.
- The N-S light will also be green when either A or B is occupied while C and D are both vacant.
- The E-W light will be green when no vehicles are present. Using the sensor outputs A, B, C and D as inputs, N-S and E-W be two outputs that go high when the corresponding light to be green. Simulate the above scenario using decoders.

A2)

AIM:


To obtain a circuit to solve the traffic light problem.

TRUTH TABLE:


TRAFFIC LIGHT PROBLEM					
INPUT				OUTPUT	
A	B	C	D	E/W	N/S
0	0	0	0	1	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	1	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	0	1	0	1
1	1	1	0	0	1
1	1	1	1	1	0

DESIGN:

 This can be designed using a 4-to-16 Decoder and simple OR Gates in the following manner:



SCREENSHOTS:

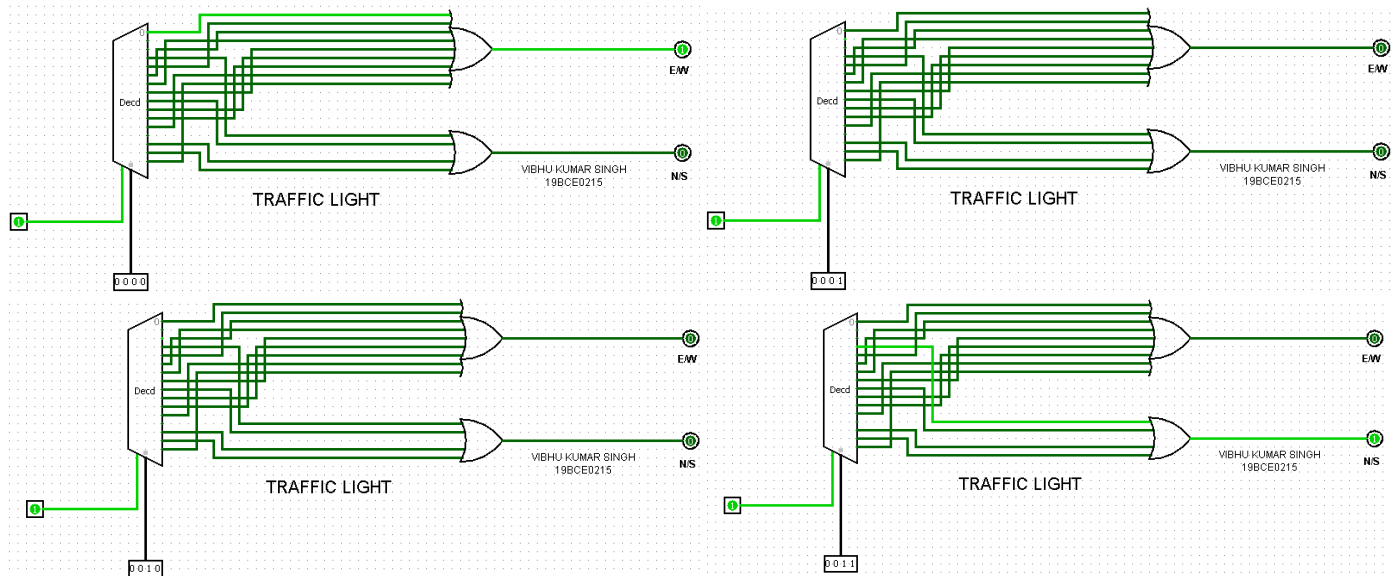

Q3) Show how two 4-to-1 and one 2-to-1 multiplexers could be connected to form an 8-to-1 MUX with three control inputs.

A3)

AIM:


To design 8-to-1 MUX using two 4-to-1 and one 2-to-1 MUX.

TRUTH TABLE:


8-TO-1 MUX			
INPUT			OUTPUT
A	B	C	
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

DESIGN:

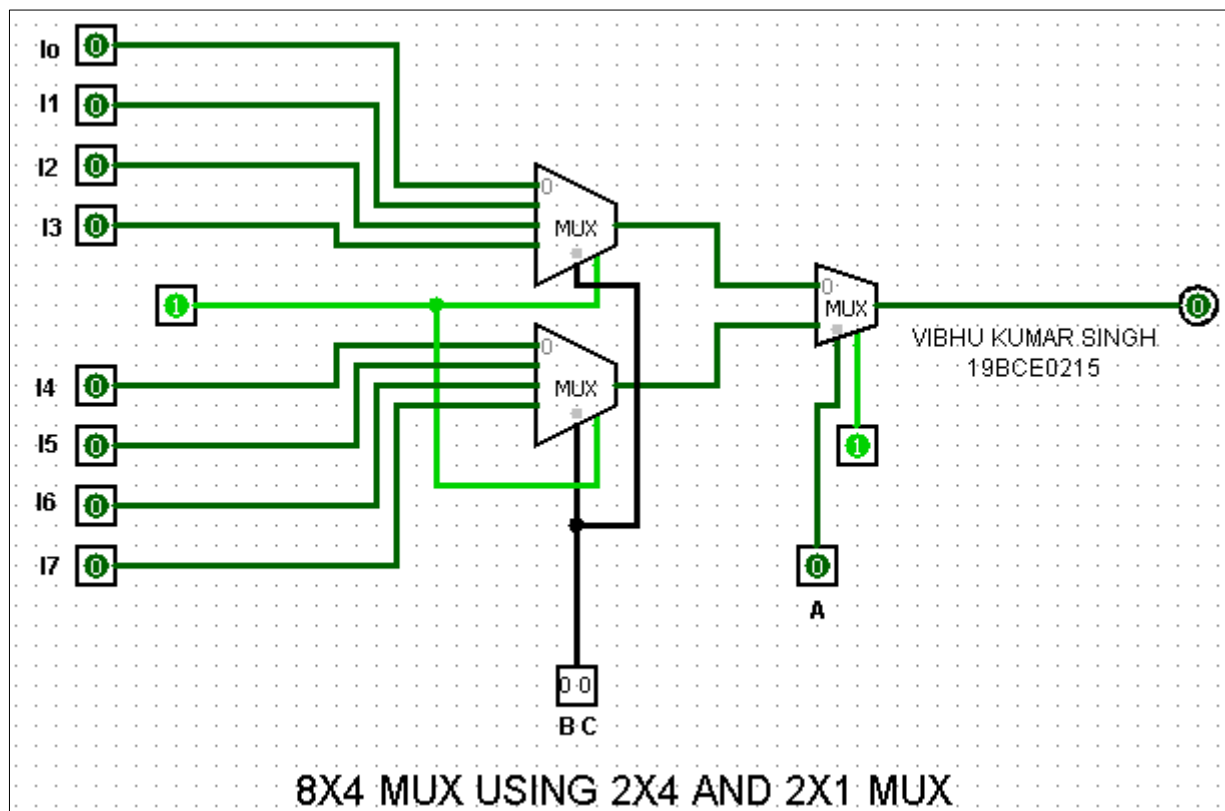
The 8-to-1 MUX using two 4-to-1 and one 2-to-1 MUX can be made like this:




SCREENSHOTS(4):

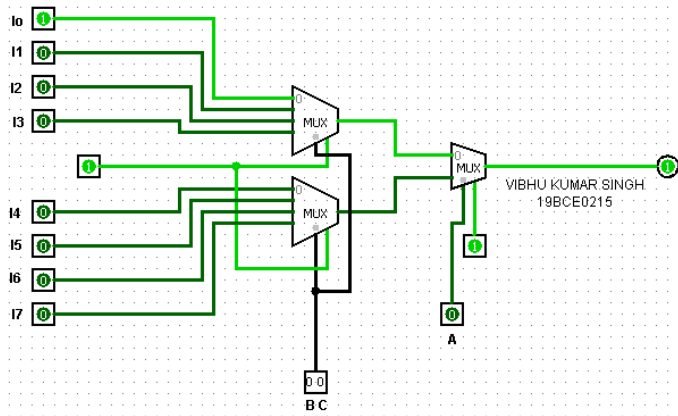


8X4 MUX USING 2X4 AND 2X1 MUX

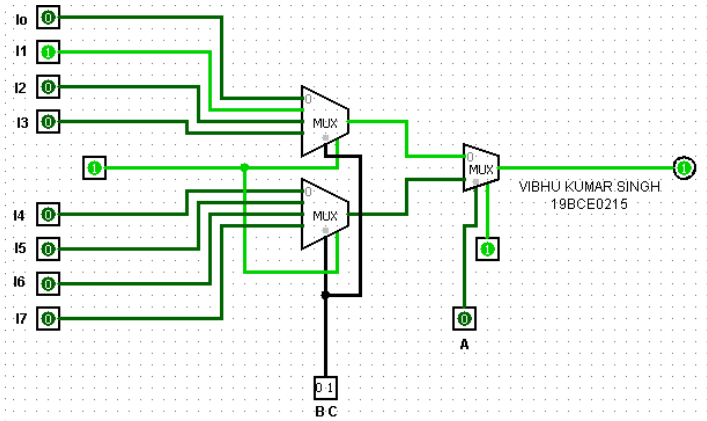

8X4 MUX USING 2X4 AND 2X1 MUX

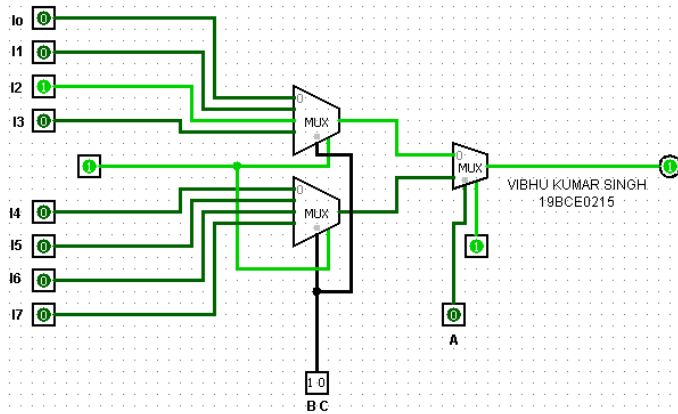

8X4 MUX USING 2X4 AND 2X1 MUX

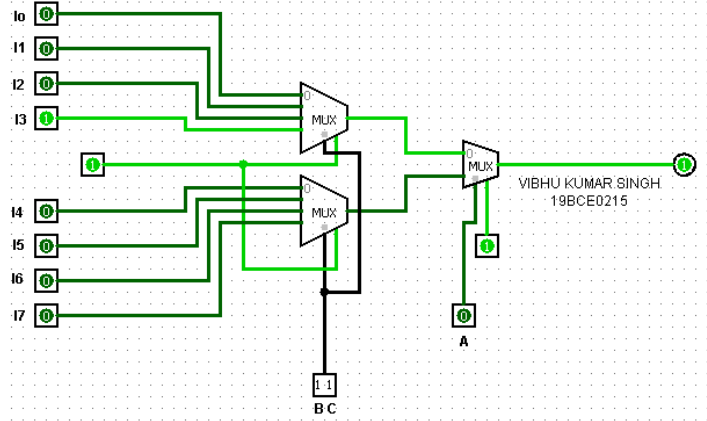

8X4 MUX USING 2X4 AND 2X1 MUX

Q4) Design a 4-bit Even parity Checker using a multiplexer.

A4)

AIM:

To design a 4-bit Even Parity Checker using a multiplexer.

TRUTH TABLE:

EVEN PARITY CHECKER				
INPUT				OUTPUT
A	B	C	D	EVEN PARITY CHECKER
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

DESIGN:

We will use reduced MUX to obtain the minimum number of input variables.

MINTERMS:


$$\text{PARITY CHECKER}(A,B,C,D)=\sum m(1,2,4,7,8,11,13,14)$$

Select lines
Input variable

MAPPING MINTERMS:

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
A'	0	①	②	3	④	5	6	⑦
A	⑧	9	10	⑪	12	⑬	⑭	15
	A	A'	A'	A	A'	A	A	A'

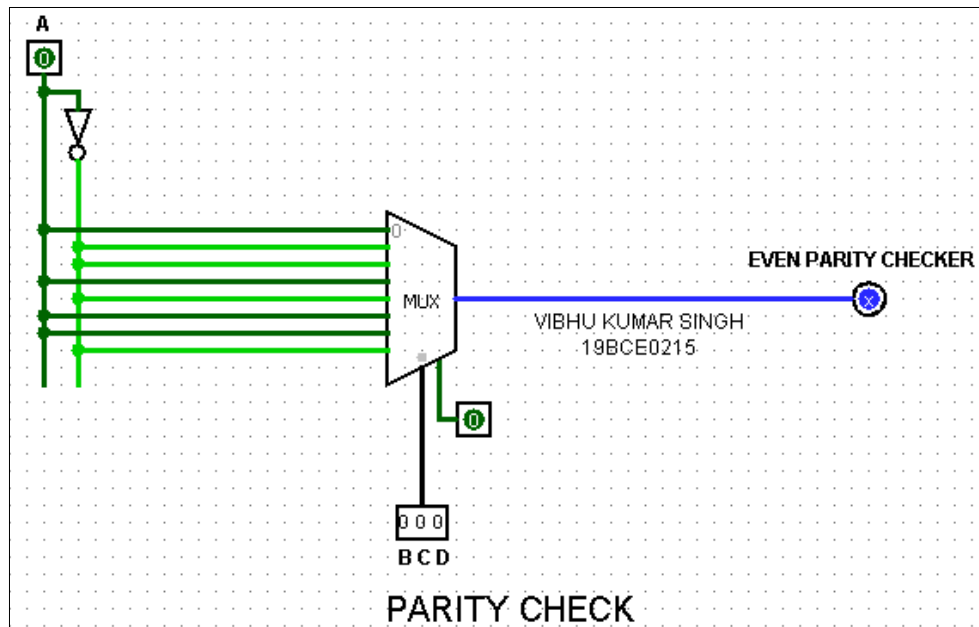The circuit for a 4-bit Even Parity Checker using a multiplexer is:



SCREENSHOTS(4):

